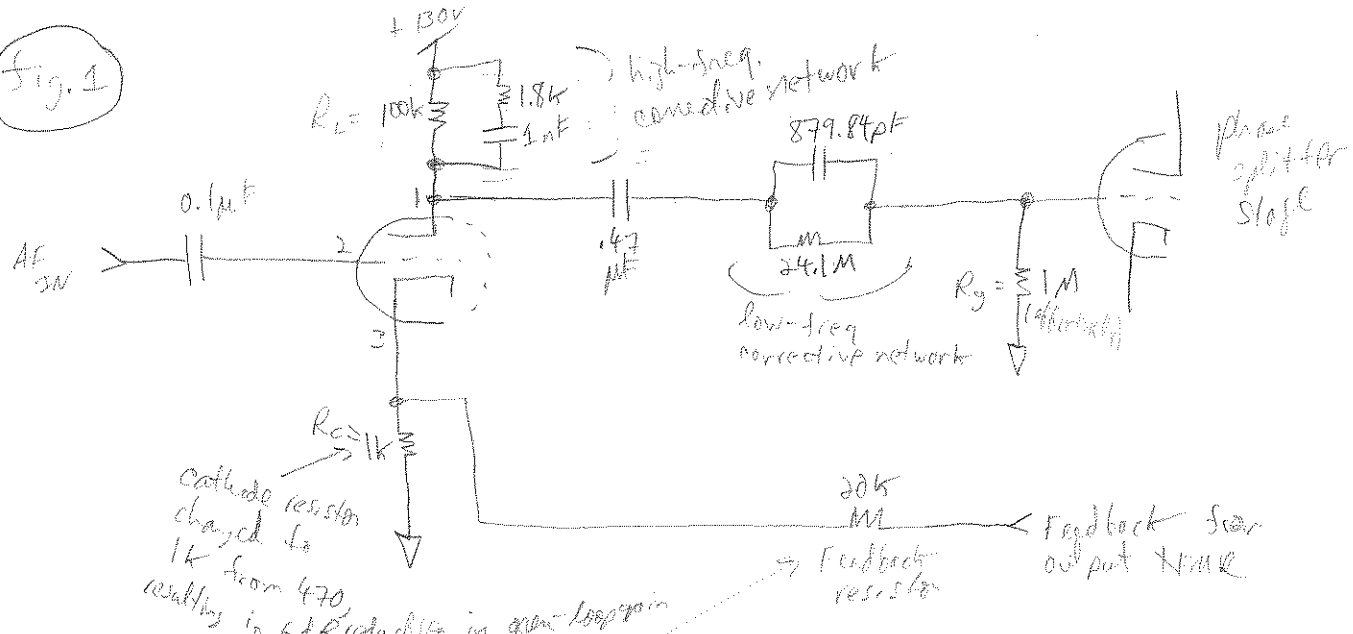


Corrective Networks 4/4/09

- applied to the first stage
- also, increase the cathode resistor on 1st stage to 1k, because the open-loop gain at mid-freq is way too high! (45dB >)
- this will drop it by 6dB

Fig. 1




- also, increase the feedback resistor to 10k, we have lots of freq BW and FWD gain, might as well use it so that the PA can output max power

- let's check the math

- according to Radio Designer's Handbook, 4th ed by F. Langford-Smith, p. 371, fig 2.59A, B

- for a high frequency corrective network:

Fig. 2

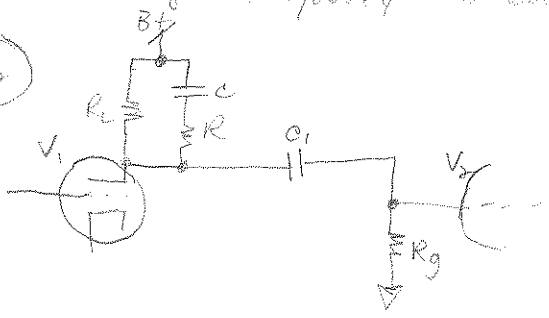

- the ultimate attenuation of the stage in dB is given by:

$$att_{in} \approx 20 \log \left(\frac{R_1 + R}{R} \right) \quad (1)$$

- when R_1 is given by:

$$R_1 = \frac{R_L R_g}{R_L + R_g} \quad (2)$$

- the cut-off freq: $f_1 = \frac{1}{2\pi R_1 C}$ (3)

- the flattening-out freq: $f_2 \approx \frac{1}{2\pi R C}$ (4)

continued on p. 2

$$V_{in} = 100\text{mV (R-R)}$$

{ ~~518.65W~~ peak output power measured into an 8Ω load resistor w/o operating in open-loop }

$$R_L = 9.6\ \Omega \Rightarrow V_{peak} = 453.75\text{V}$$

$$V_{peak} = 66\text{V}$$


- all of this data was plotted in tube-bode-plots.m

- open-loop gain before corrective networks

f(Hz)	Vout (R-R)	Phase (deg)
1		
2		
3	0.574	27
4	1.08	21.6
5	1.69	14.4
6	2.36	17.2.8
7	3.12	191.52
8	3.96	14.4
9	4.72	14.56
10	5.55	129.6
20	11.7	29.2
30	15.2	64.8
40	17.10	51.84
50	18.20	36
60	18.35	32.40
70	18.90	32.76
80	19.25	25.92
90	19.4	25.9
100	19.4	18
200	20.2	14.4
300	20.2	8.64
400	20.2	0
500	20.2	0
600	20.2	0
700	20.2	0
800	20.2	0
900	20.20	0
1000	20.15	0
2000	"	"
3000	"	"
4000	20.7	"
5000	"	18
6000	"	21.6
7000	"	25.2
8000	"	23.04
9000	21.35	19.44
10000	21.75	18
20k	20.95	43.2
30k	14.75	25.6
40k	11.6	57.6
50k	14.25	81
60k	12.5	86.4
70k	9.95	100.8
80k	8	115.2
90k	6.85	243
100k	5.85	117.4

This is OPEN-LOOP Bode Plot Data

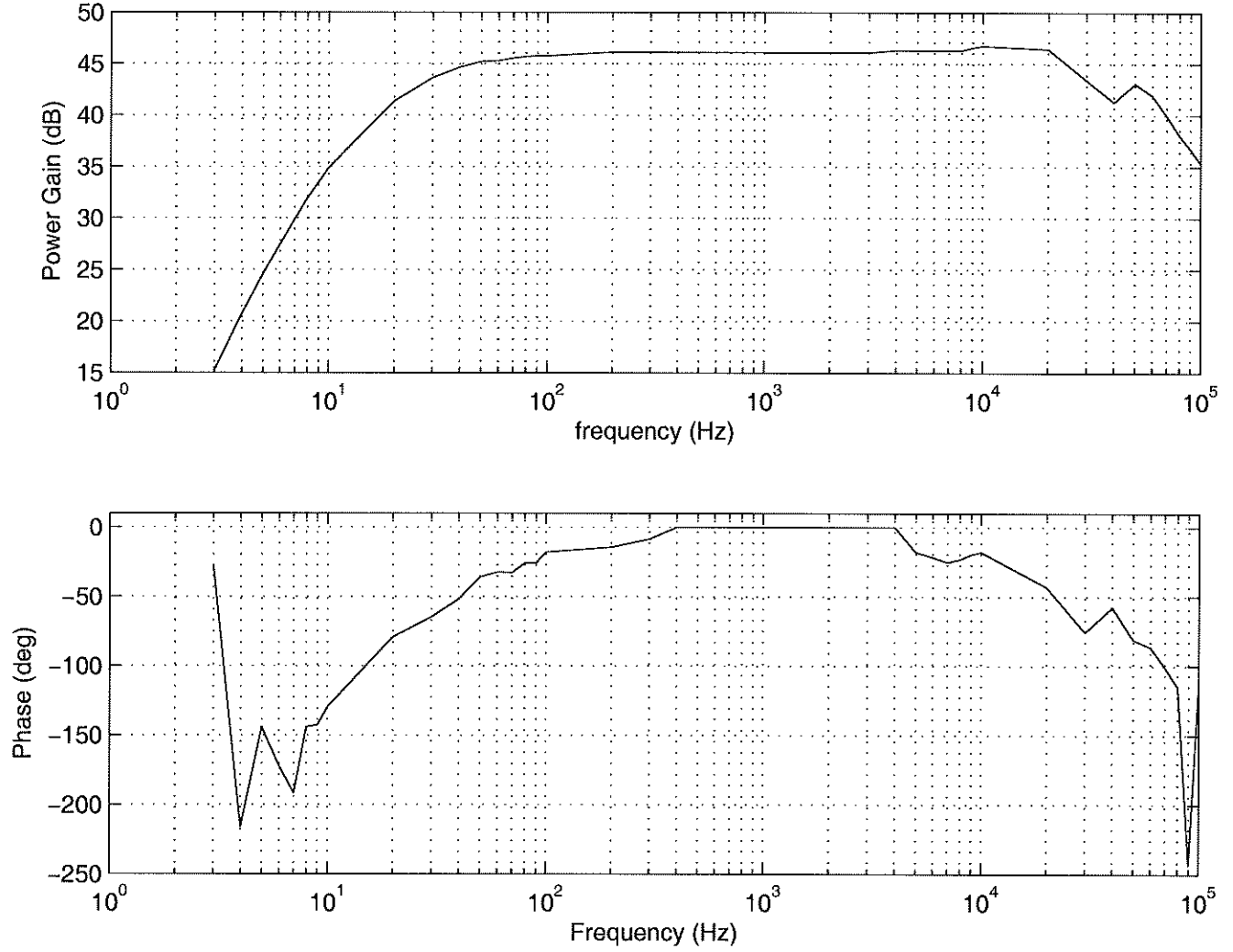Open-Loop Bode Plot Before Corrective Networks



- looking at eq ① solve for R, so we can work towards the paper attenuation

$$\text{attn} = 20 \log \left(\frac{R_1 + R}{R} \right)$$

$$\frac{\text{attn}}{20} = \log \left(\frac{R_1 + R}{R} \right)$$

$$10^{(\text{attn}/20)} = \frac{R_1 + R}{R}$$

$$10^{(\text{attn}/20)} = \frac{R_1}{R} + 1$$

$$10^{(\text{attn}/20)} - 1 = \frac{R_1}{R}$$

$$\Rightarrow R = \frac{R_1}{10^{(\text{attn}/20)} - 1} \quad \textcircled{5}$$

- solve for C using eq ④

$$f_2 = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi R f_2} \quad \textcircled{6}$$

- estimate f_2 off of the bode plot using data from p.1a.
 $\rightarrow f_2$ is the ^{high} freq where the phase hits 180° , on the upper, higher freq, portion of the plot

$$f_2 \approx 85 \text{ kHz} \quad \checkmark \text{ due to increased } \text{attn} \text{ caused by resistor in that stage} = 3 \text{ dB in this case}$$

$$\text{attn} \approx 37.4 - 6 = 31.4 \text{ dB} + \text{gain margin}$$

- eq's 5, 6, 2, 3, and 4 were coded up into tlcx-bode-plot.m with the values above and with the values in (fig 1) (actual schematic);


\Rightarrow the results for the high-freq noninverting network are:

$f_1 = 1.651 \text{ kHz}$	$\text{attn} = 34.4 \text{ dB}$
$f_2 = 85 \text{ kHz}$	$R = 1.7659 \text{ k}$
	$C = 1060 \text{ pF}$

\rightarrow these results are applied to fig 1

- for a low freq. corrective network:

fig. 3

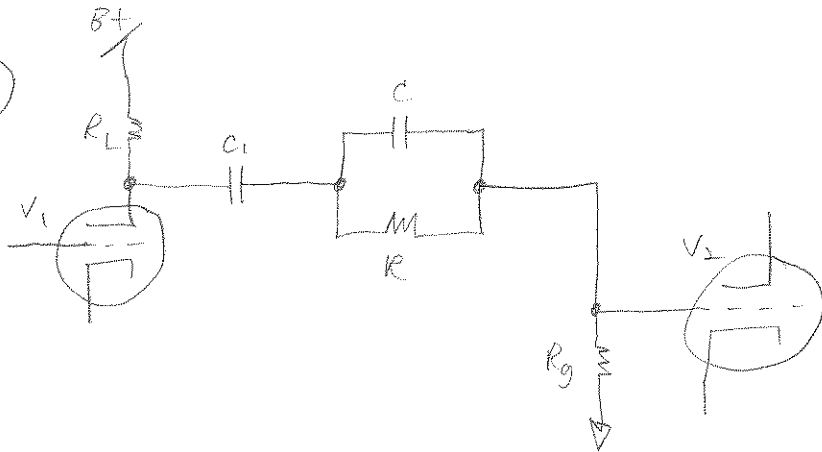

- the ultimate attenuation of the step in dB is

$$\text{attn} \approx 20 \log \left(\frac{R + R_g}{R_g} \right) \quad (7)$$

- the cut-off freq: $f_1 = \frac{1}{2\pi C(R_L + R_g)}$ (8)

- the flattening-out freq: $f_2 \approx \frac{1}{2\pi RC}$ (9)

- using eq (7), solve for R

$$\text{attn} = 20 \log \left(\frac{R + R_g}{R_g} \right)$$

$$\frac{\text{attn}}{20} = \log \left(\frac{R + R_g}{R_g} \right)$$

$$10^{\frac{(\text{attn}/20)}{10}} = \frac{R + R_g}{R_g}$$

$$10^{\frac{(\text{attn}/20)}{10}} = \frac{R}{R_g} + 1$$

$$10^{\frac{(\text{attn}/20)}{10}} - 1 = \frac{R}{R_g}$$

$$\Rightarrow R = R_g \left[10^{\frac{(\text{attn}/20)}{10}} - 1 \right] \quad (10)$$

- using eq. ⑨ solve for C

$$f_2 = \frac{1}{2\pi RC} \Rightarrow C = \frac{1}{2\pi R f_2} \quad \text{⑪}$$

- estimate f_2 , where the lower end of the bode plot (from data on p. 1a) hits 180°

$f_2 \approx 7.5 \text{ Hz}$ due to increased cathode resistance on 2nd stage

$\text{attn} = 31 - 6 = 25 + \frac{3}{2} = 28$

↑ gain margin of 3dB

- eq's 10, 11, 8, and 9 were coded up in to MATLAB, file name tube_bode_plots.m, f_2 and attn were inputted, resulting in:

$f_1 = 164.5 \text{ Hz}$	$\text{attn} = 28 \text{ dB}$
$f_2 = 7.5 \text{ Hz}$	$R = 24.1 \text{ M}$
	$C = 879.84 \text{ pF}$

↳ these results are applied to fig 1

- another option is to reduce the grid resistor in the 2nd stage and try to achieve more conservative R, C values for the corrective networks


- let $R_g = 100k$

- and, let the cathode resistor in the 1st stage, R_c , be $470 = R_c$

\Rightarrow \approx dB lower fwd loop gain (same as if $R_c = 1k$)

\Rightarrow reduce feedback resistor to $10k$

- re-draw here (actual values)

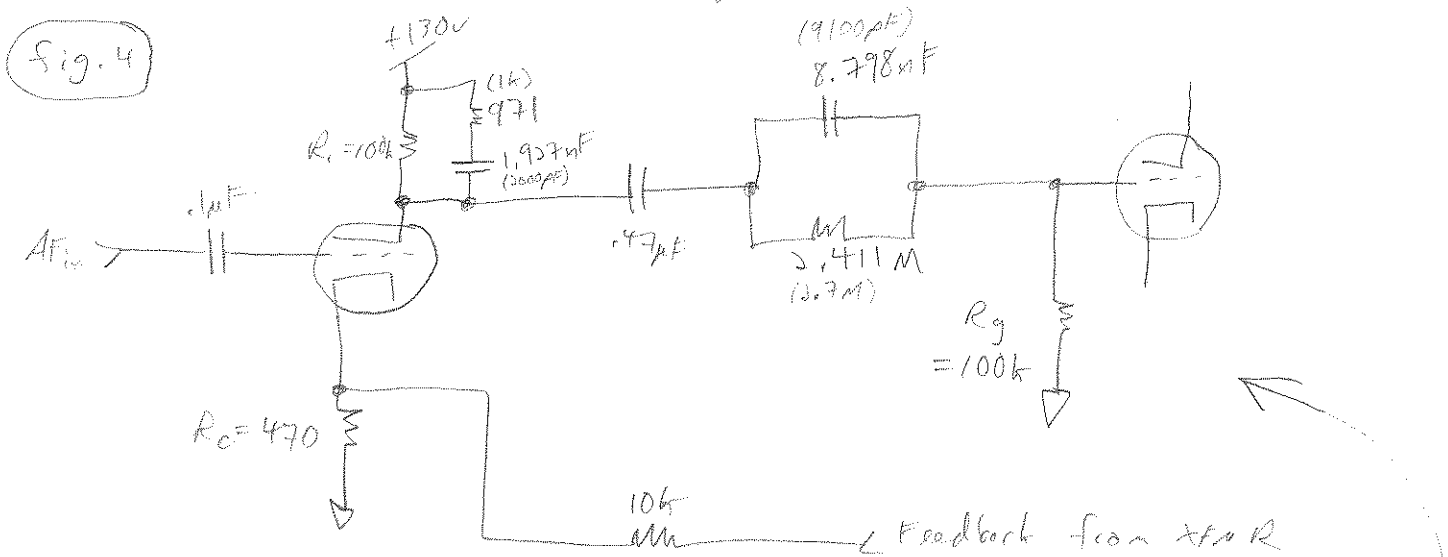

- apply the new values of R_g to the .sm file, resulting in:

High-Freq Network: $f_1 = 1.651 kHz$
 $f_2 = 85 kHz$
 $R = 0.971 k$
 $C = 1.927 nF$

Low-Freq Network: $f_1 = 90.44 Hz$
 $f_2 = 7.5 Hz$
 $R = 2.4119 M$
 $C = 8.7984 nF$

apply these to Fig. 4

$$V_{in} = 100 \text{ mV } (\rho - \rho)$$

f(Hz)	Vout (p-p)	Phase (deg)
3		
4	0.365	-158
5	0.272	-162
6	0.375	-151.2
7	0.494	-138.6
8	0.624	-144
9	0.766	-145.8
10	0.932	-126
20	2.67	-117
30	4.55	-94.5
40	6.28	-86.4
50	7.78	-81
60	8.9	-70.2
70	10	-63
80	10.92	-57.6
90	11.68	-48.6
100	12.12	-45
200	14.68	-21.6
300	15.24	-10.8
400	15.34	0
500	15.34	+4.5
600	14.98	+10.8
700	14.84	+15.12
800	14.56	21.6
900	14.26	24.3
1E3	13.82	+27
2E3	10.72	+46.8
3E3	8.24	+54
4E3	6.66	+72
5E3	5.42	+72
6E3	4.63	+75.6
7E3	4.01	+75.6
8E3	3.53	+79.2
9E3	3.145	+81
10E3	2.845	+81
20E3	1.465	+90
30E3	0.858	+108
40E3	0.533	+72
50E3	0.613	+90
60E3	0.538	+97.2
70E3	0.433	+107.1
80E3	0.356	+115.2
90E3	0.300	+113.4
100E3	0.249	+117
200E3	6.2E-3	+122.4
300E3	33.7E-3	+108
400E3	23.1E-3	+108
500E3	146.5E-3	+72
600E3	171.5E-3	+75.6
700E3	159E-3	+75.6
800E3	146E-3	+72
900E3	148E-3	+81
1E6	165E-3	+72

V_{in} changed to 200 mV (p-p)

V_{in} changed to 800 mV (p-p)

Bode Plot Data

- open-loop gain
- after correction networks from fig 4, were installed

$$\text{Max } V_{pp} @ 1 \text{ kHz} = 67.6 \text{ V}$$

$$R_L = 9.6 \Omega$$



$$\Rightarrow P_{peak} = 4.76 \text{ W}$$

as observed:

(+) \Rightarrow output is leading input

(-) \Rightarrow output is lagging input

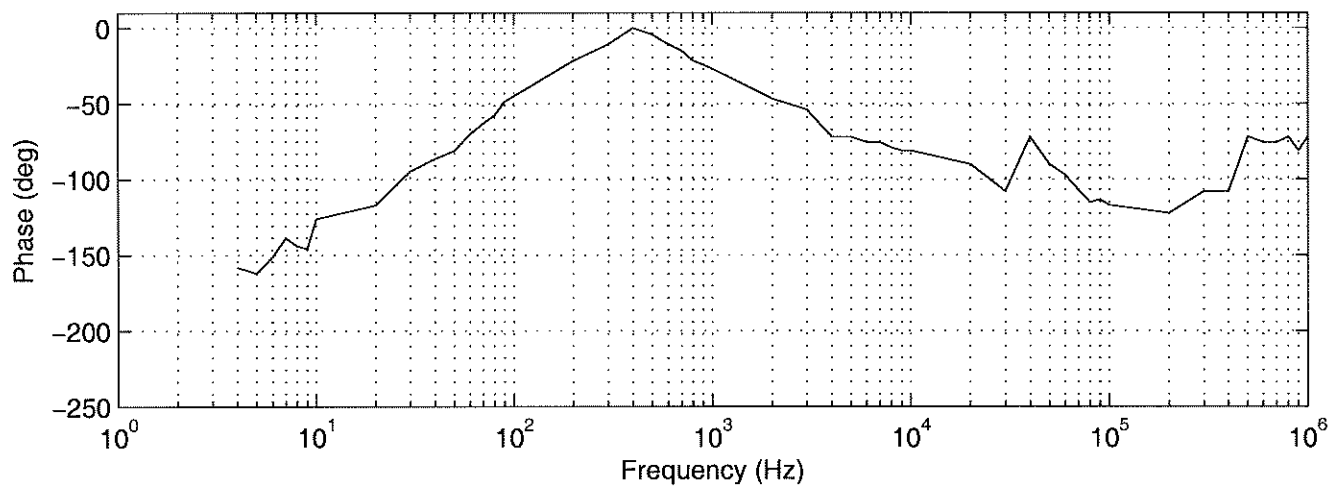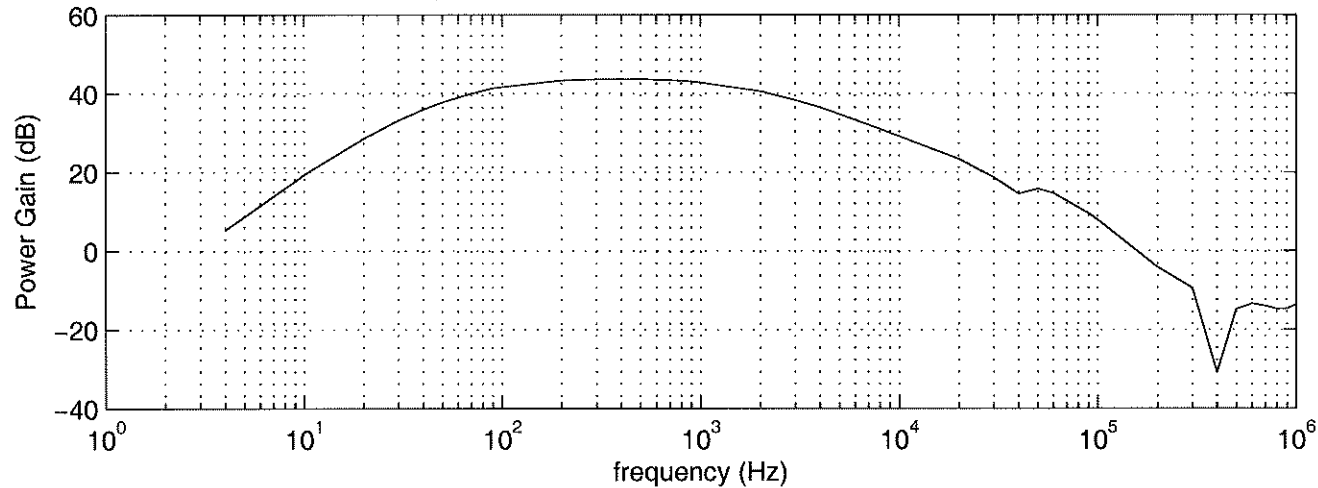Open-Loop Bode Plot After Corrective Networks



- closed-loop data, $V_{in(p-p)} = 400mV$
 $R_{feedback} = 10k$



f (Hz)	$V_{out(p-p)}$	Phase (deg)
5	0.990	-135
6	1.37	-129.6
7	1.715	-126
8	2.65	-115.2
9	2.42	-113.4
10	2.81	-108
20	6.12	-79.2
30	7.86	-54
40	8.78	-43.2
50	9.34	-36
60	9.56	-32.4
70	9.70	-25.2
80	9.82	-21.6
90	9.9	-19.44
100	9.9	-18
200	10.1	-7.2
300	10.1	-5.4
400	10.1	0
500	10.1	0
600	10.1	0
700	10.1	0
800	10.1	0
900	10.14	0
1k	10.1	10.3
2k	10.06	7.2
3k	9.82	13.5
4k	9.68	21.6
5k	9.30	27
6k	9.02	32.4
7k	8.66	31.5
8k	8.32	36
9k	8.0	40.5
10k	7.76	45
20k	5.11	72
30k	3.3	86.4
40k	2.3	72
50k	2.53	81
60k	2.24	97.2
70k	1.805	100.8
80k	1.505	115.2
90k	1.248	113.4
100k	1.054	113.4
200k	0.251	108
300k	0.135	108

load
 Resistor
 $R_L = 9.6k$

$V_{pp(max)} = 68.2$ at 14Hz
 $V_{pp(max)} = 63.4$ at 50Hz
 $V_{pp(max)} = 73.0$ at 10kHz
 $V_{pp(max)} = 58.2$ at 15kHz
 $V_{pp(max)} = 47.2$ at 10Hz
 $V_{pp(max)} = 64.2$ at 20Hz

$R_{feedback} = 10k$

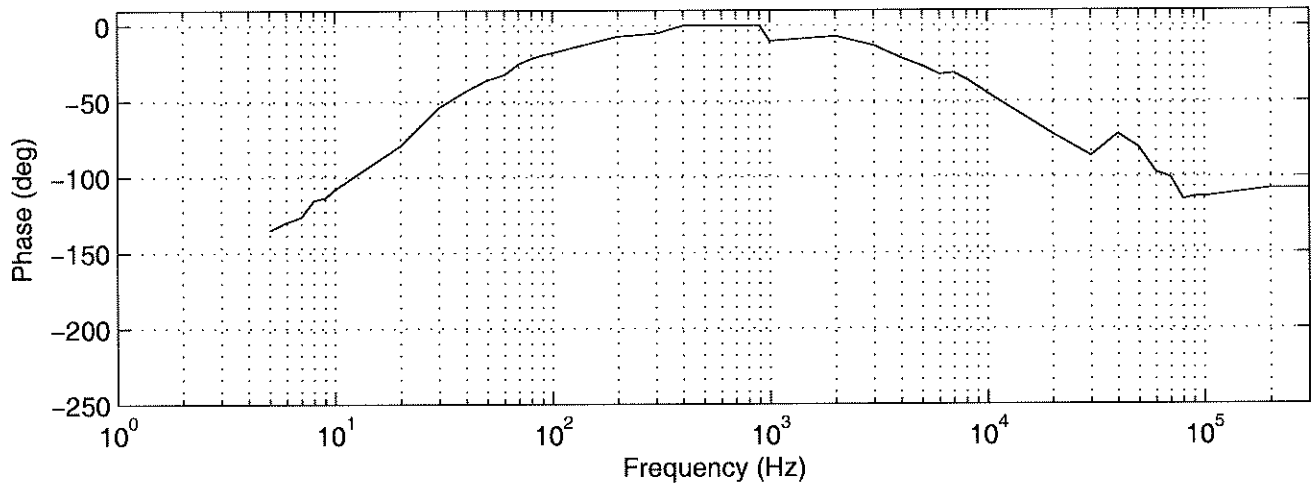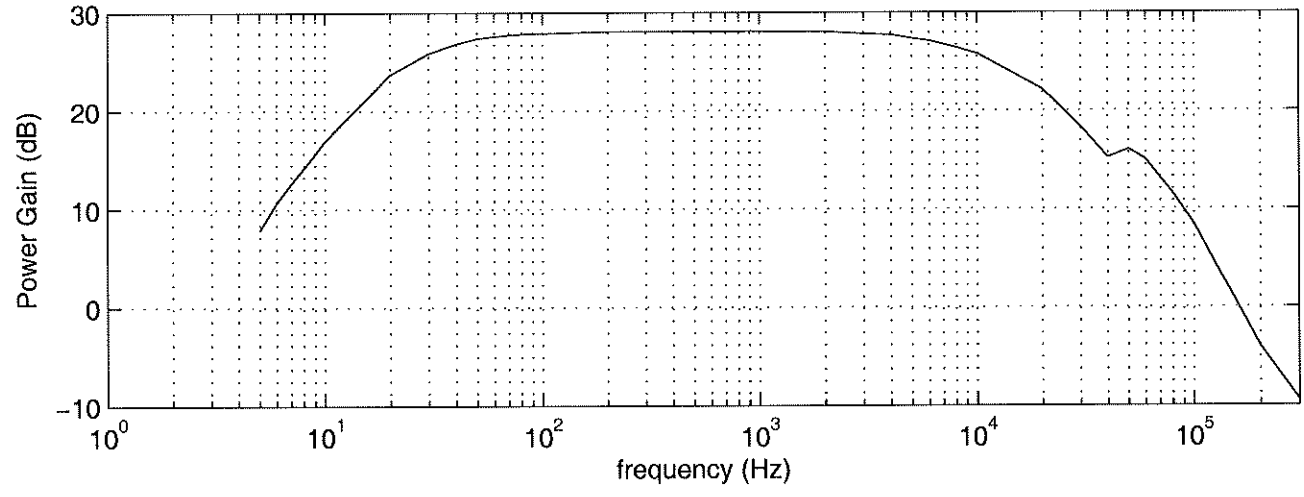Closed-Loop (10K feedback resistor) Bode Plot After Corrective Networks



→ closed-loop data, $V_{in}(p-p) = 400\text{ mV}$, $R_{load} = 4.7\text{ k}\Omega$

$f(\text{Hz})$	$V_{out}(p-p)$	Phase (deg)	$f(\text{Hz})$	Max Power Out	Vpp (peak)
5	0.888	-135	10	37.7	
6	1.08	-108	20	61.3	
7	1.33	-113.4	50	66.7	
8	1.56	-100.8	1E3	66.7	
9	1.8	-97.2	10E3	73.1	
10	2.03	-90	15E3	57.0	
20	3.76	-57.6			
30	4.53	-43.2			
40	4.91	-36			
50	5.13	-27			
60	5.23	-21.6			
70	5.30	-20.16			
80	5.35	-20.16			
90	5.38	-16.2			
100	5.41	-14.4			
200	5.44	-7.2			
300	5.44	-5.4			
400	5.44	-2.88			
500	5.44	0			
600	5.44	0			
700	5.44	0			
800	5.44	0			
900	5.44	0			
1E3	5.43	0			
2E3	5.43	7.2			
3E3	5.43	10.8			
4E3	5.34	14.4			
5E3	5.32	16.2			
6E3	5.25	19.44			
7E3	5.19	22.68			
8E3	5.13	25.92			
9E3	5.03	29.16			
10E3	4.94	28.8			
20E3	3.99	50.4			
30E3	2.93	70.2			
40E3	2.30	50.4			
50E3	2.575	63			
60E3	2.27	86.4			
70E3	1.89	100.8			
80E3	1.58	100.8			
90E3	1.308	110.16			
100E3	1.10	117			
200E3	0.253	115.2			
300E3	0.139	108			
400E3					
500E3					
600E3					
700E3					
800E3					
900E3					
1M					

Load
Resistor
= 9.6 Ω

Closed-Loop (4.7K feedback resistor) Bode Plot After Corrective Networks

