
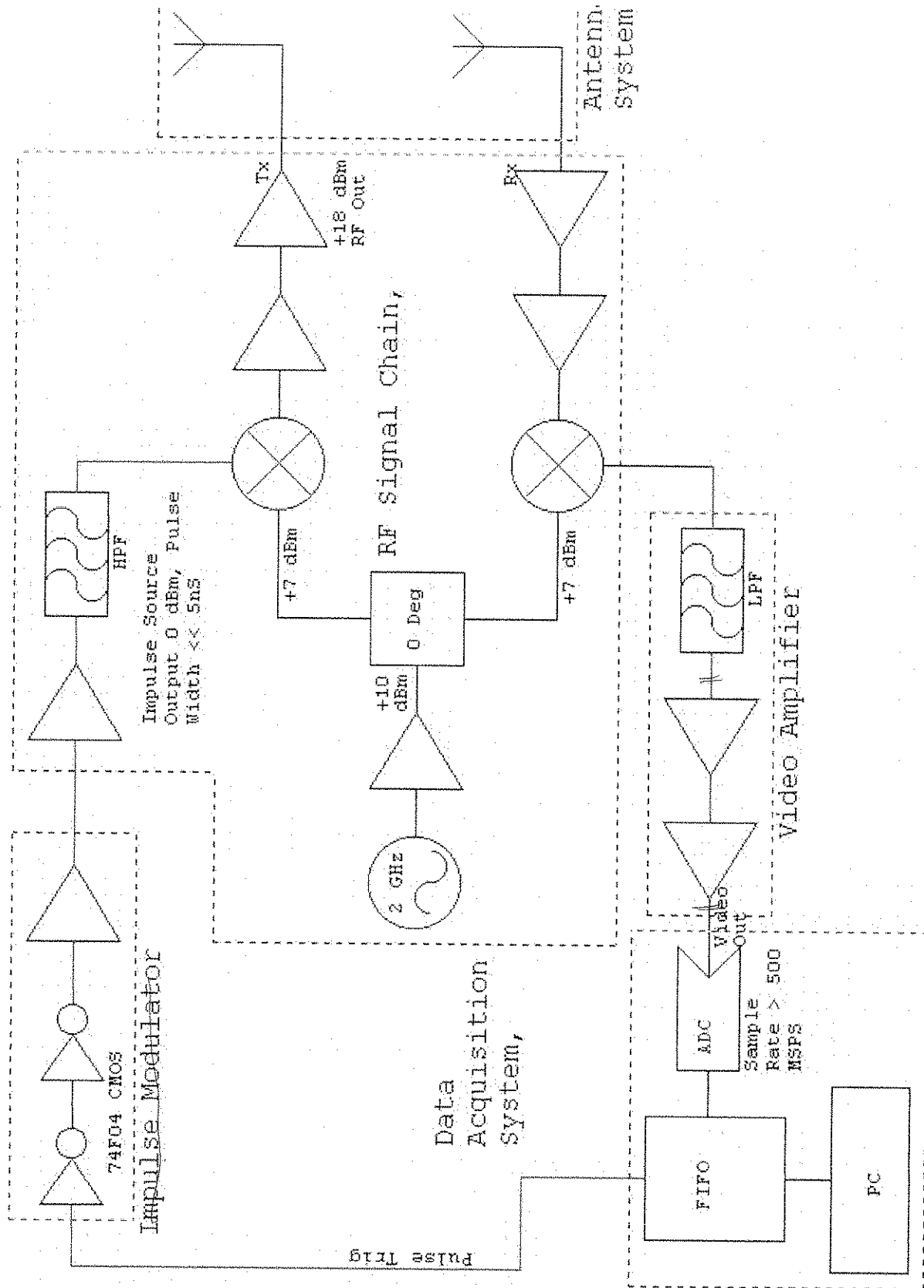




ECE 480 Project

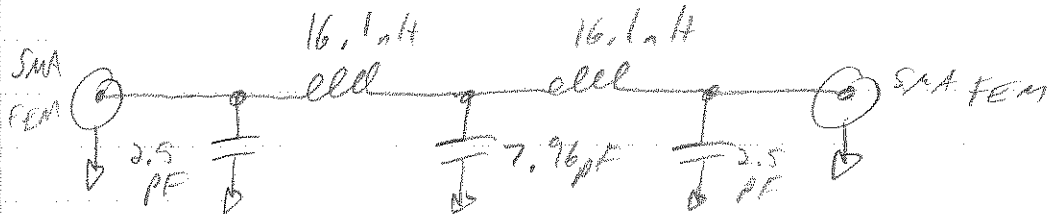




5th order Butterworth
 800 MHz LPF



IF Filter

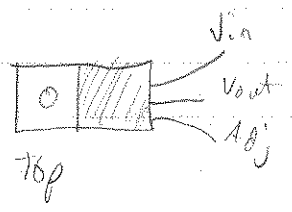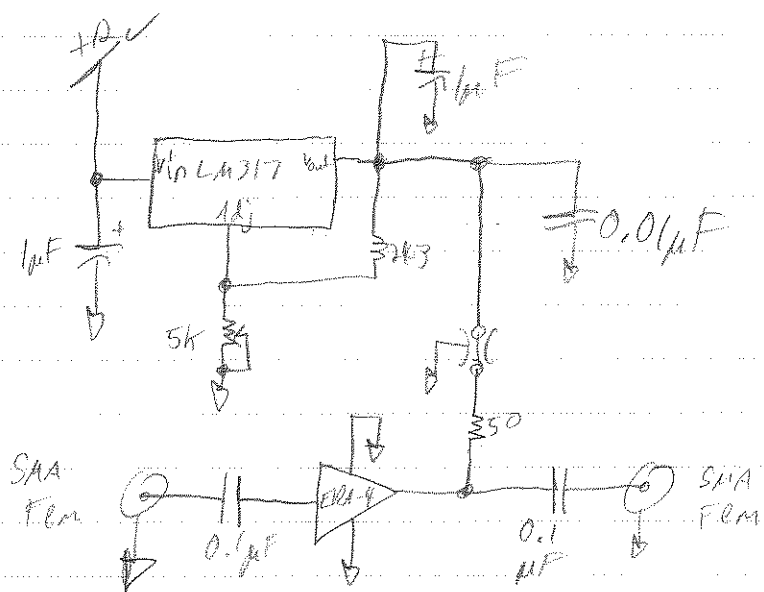



Adjustable Bias
Amp

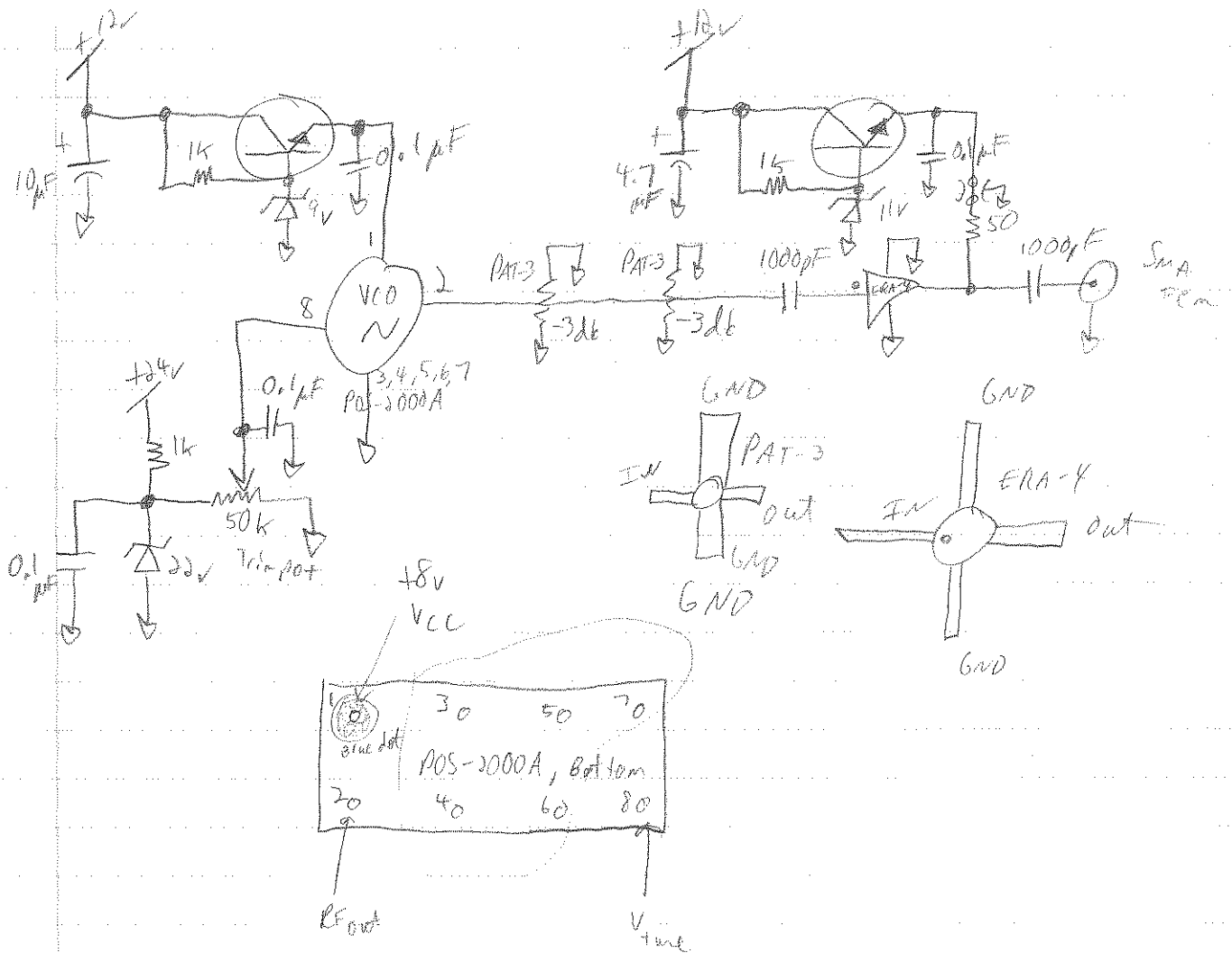

VCO
 1.5 - 2 GHz

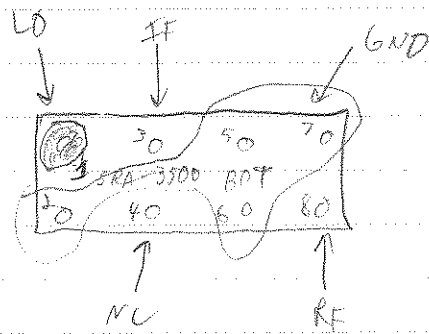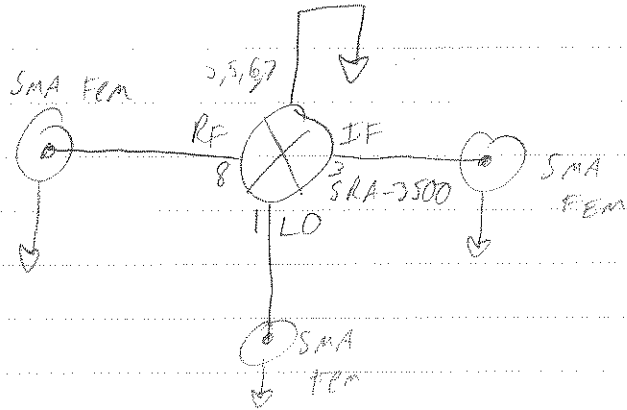

tx/Rx mixer

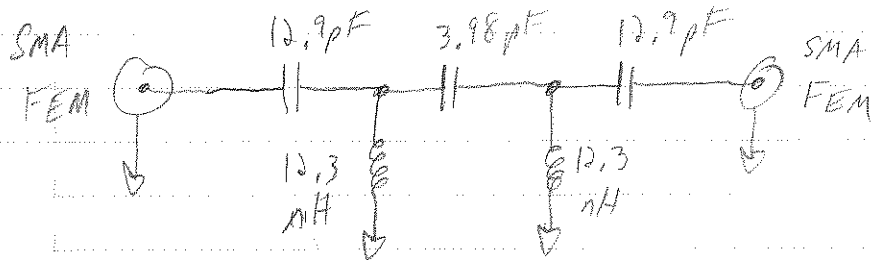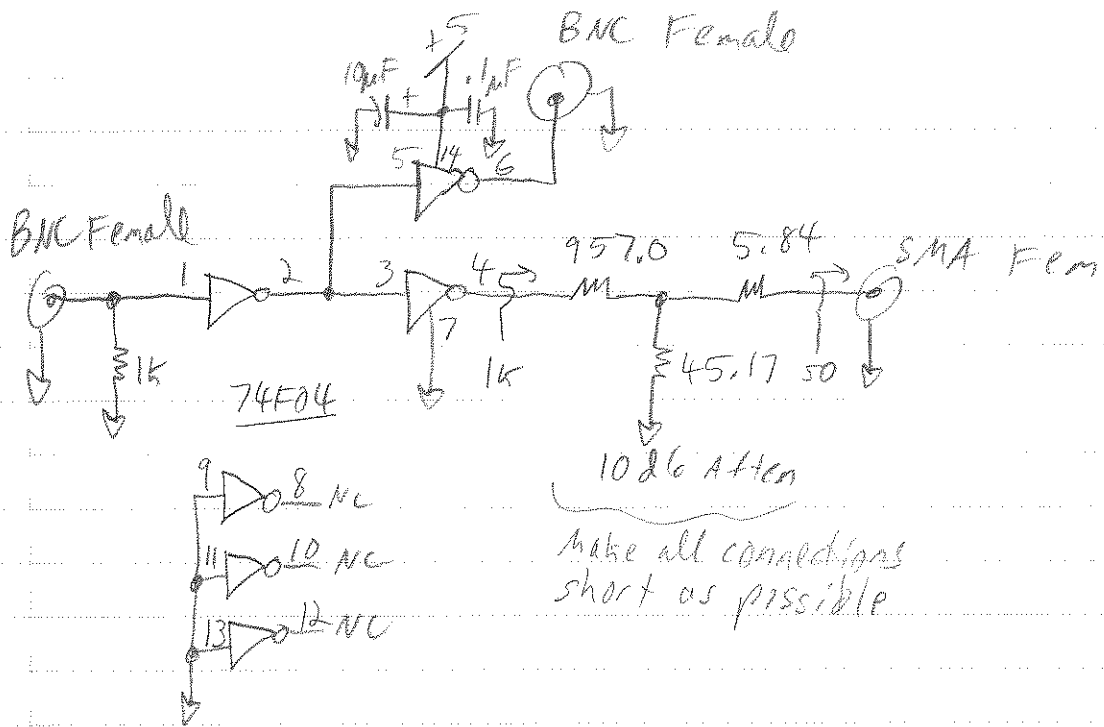


5th order 400 MHz HP
 Butterworth response
 → Build on Microstrip


Impulse
 Source

Butterworth Filter calculations


→ 400 MHz HP, 5th order

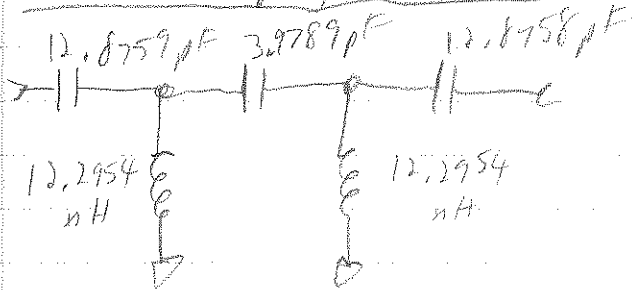


300 MHz HP, 5th order

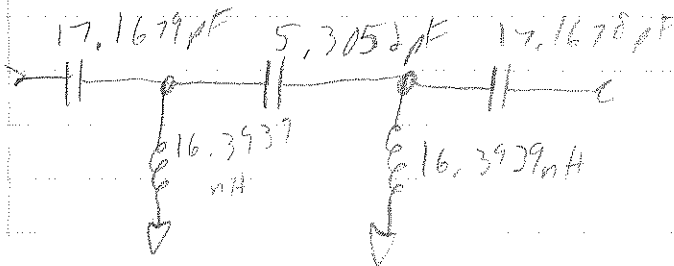

400 MHz HP, 3rd order

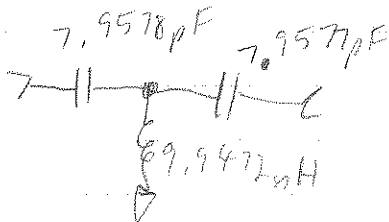

300 MHz HP, 3rd order

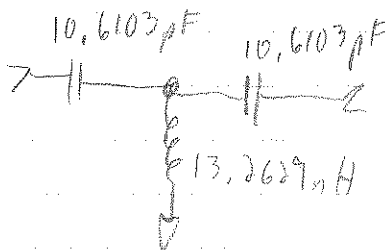

Monday, Home to solo

SPAC




at kellogg center

- 2 ZEM-4300
- 30 ERA-4
- 1 ZN2PD-96
- 5 POS-2000A

- Mixer
- Amp
- splitter
- VCO

79.95	159.90
3.85	115.5
69.95	69.95
14.95	74.75
<hr/>	
	420.10

Just need 2
Just need 10

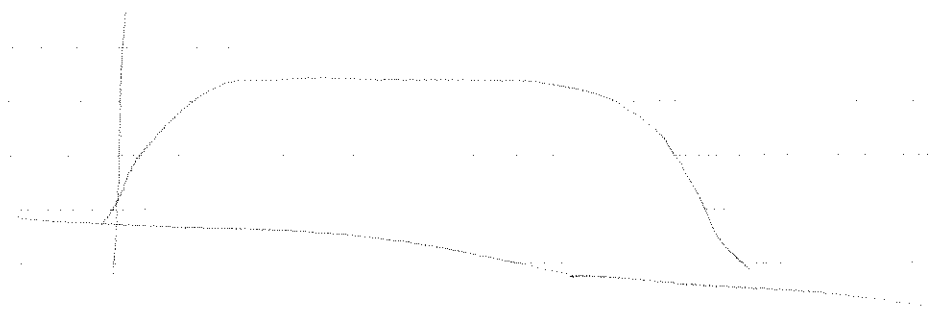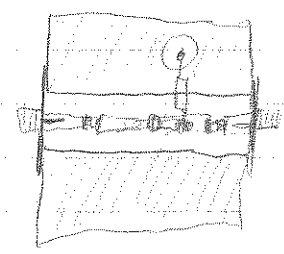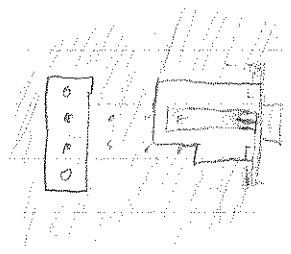

Design Specifications

Carrier freq $\approx 2.6\text{GHz}$

Pulse width $\leq 5\text{ns}$

Tx Power $+20\text{dbm}$

Coherent Radar structure




Proof of concept prototype

size, power supplies, etc not considered yet.

Budget

- Transmitter and Receiver - \$400
- Short pulse generator - \$50
- Antenna - \$25
- Video Amplifier - \$25
- Data Acquisition system - \$0
(use existing scopes in Lab)

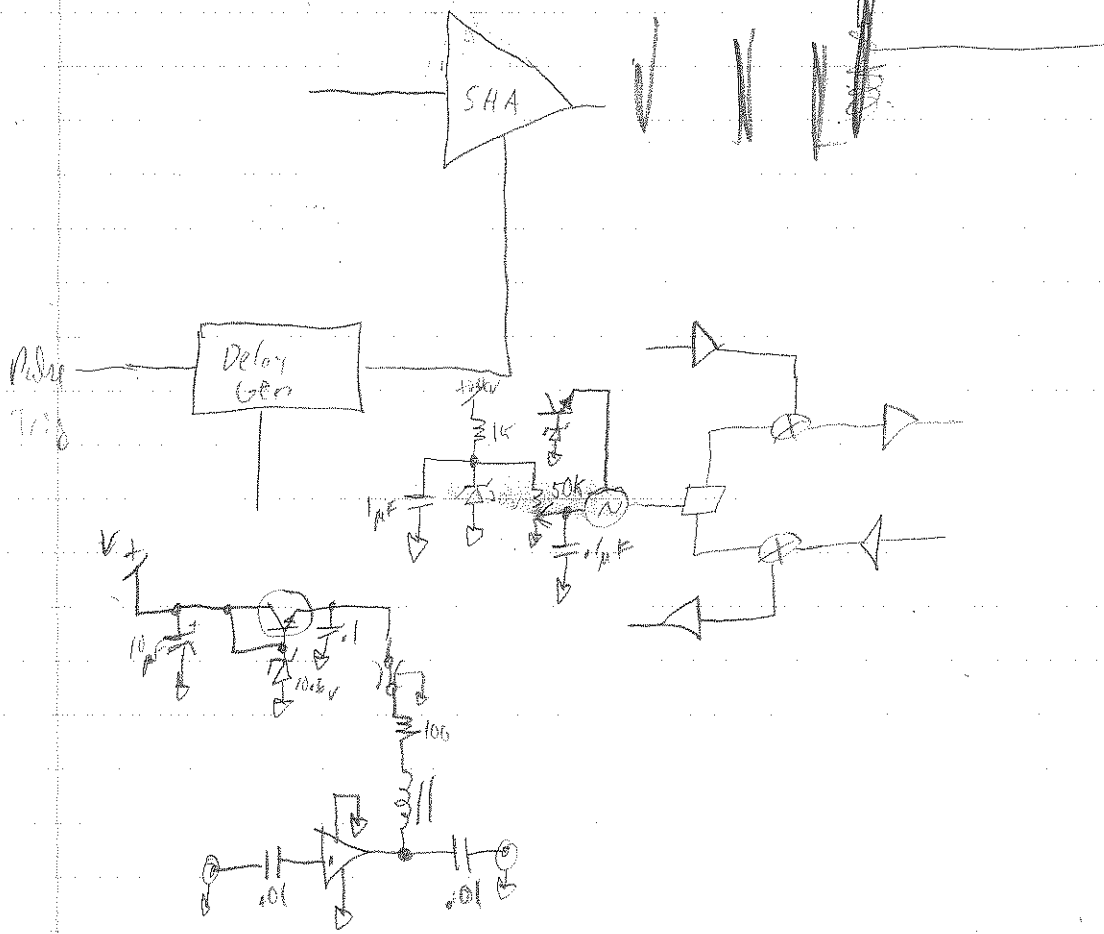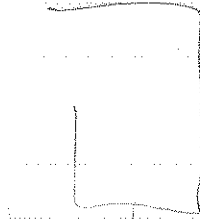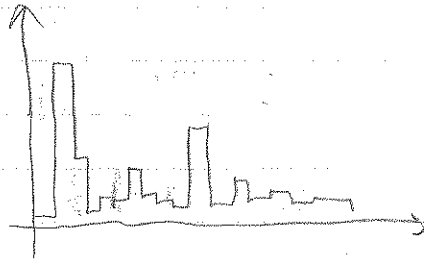- Get a project, write a small report
How solve it better.



Poc + C

<u>R17</u>	<u>R16</u>	<u>R15</u>	<u>R14</u>	<u>R13</u>	<u>R12</u>	<u>R11</u>	<u>R10</u>
0	0	0	0	0	0	1	1
0	0	0	0	0	0	0	1
					1	1	1

3

1

7

Digi-key (800) 344 4539

4	12nH Inductor	PCD1295CT-ND	1.03	4.12
4	15nH Inductor	PCD1296CT-ND	1.03	4.12
4	22nH Inductor	PCD1298CT-ND	1.03	4.12

10	2.7pF cap	399-1005-1-ND		0.66
10	3.3pF cap	399-1007-1-ND		0.66
10	8.2pF cap	399-1009-1-ND		3.41
10	10pF cap	399-1011-1-ND		0.65
10	12pF cap	399-1013-1-ND		0.68


22 SMA Female connector J493-ND 4.71 103.62

10	11v zener	1N5241BDICT-ND		2.10
1	8.7v zener	1N5238BDICT-ND		0.38
1	22v zener	1N5251BDICT-ND		0.38

Surplus sales of Nebraska (402) 346-4750

7 Feed through capacitor (FRI) 514CJ 3.50

26

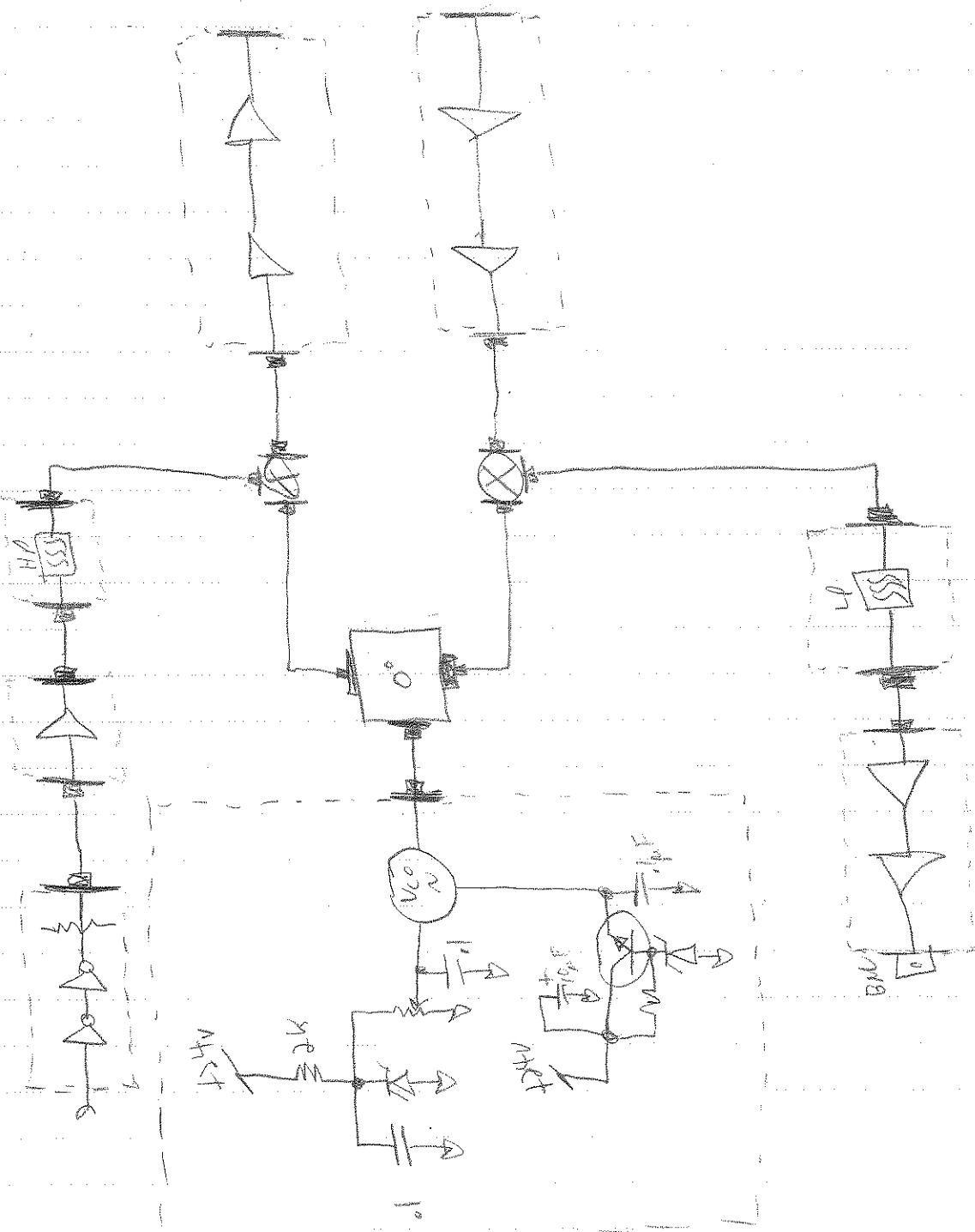



Antenna

- 2 weeks after break

Short pulse


- 3 weeks after break

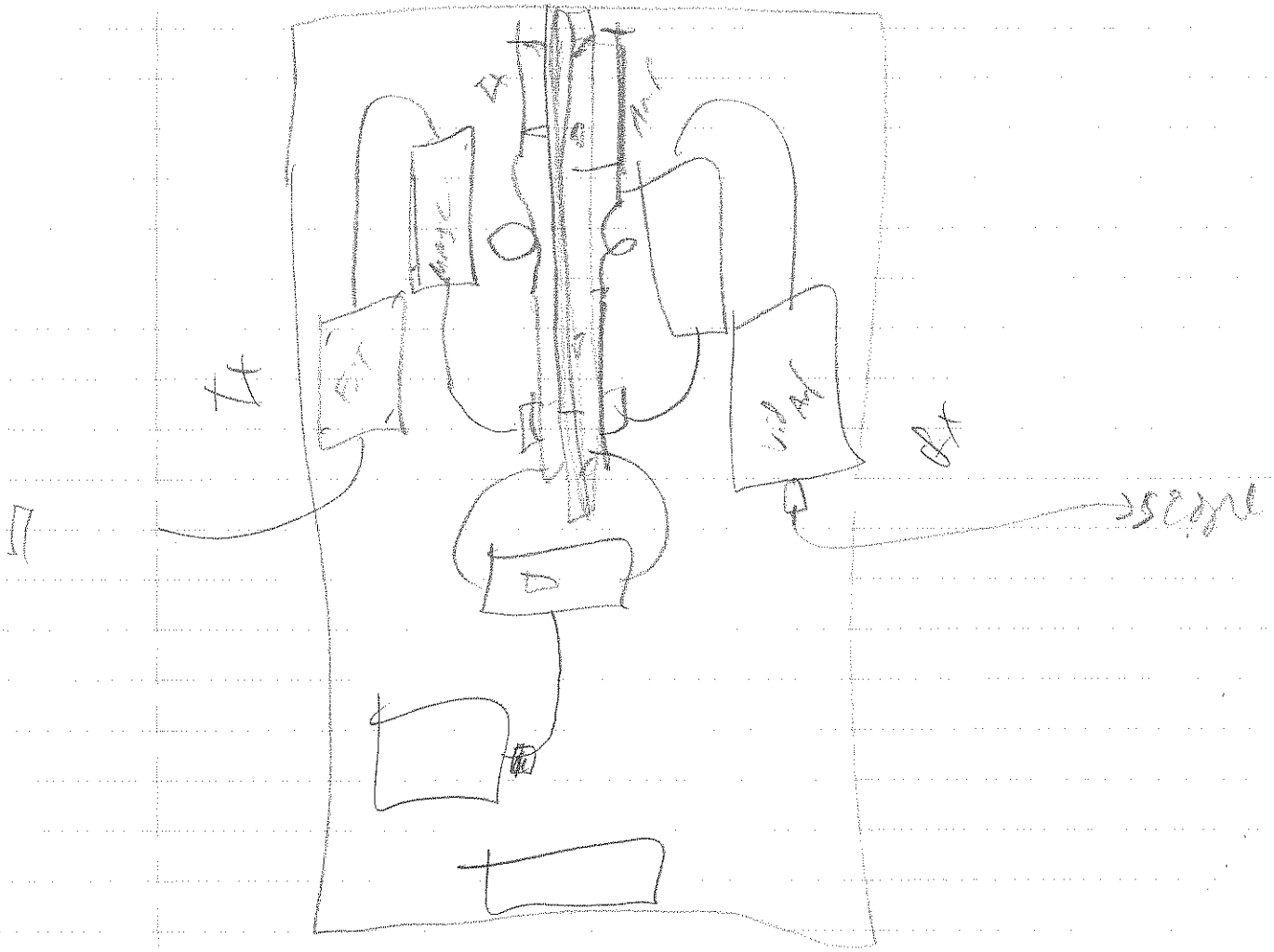


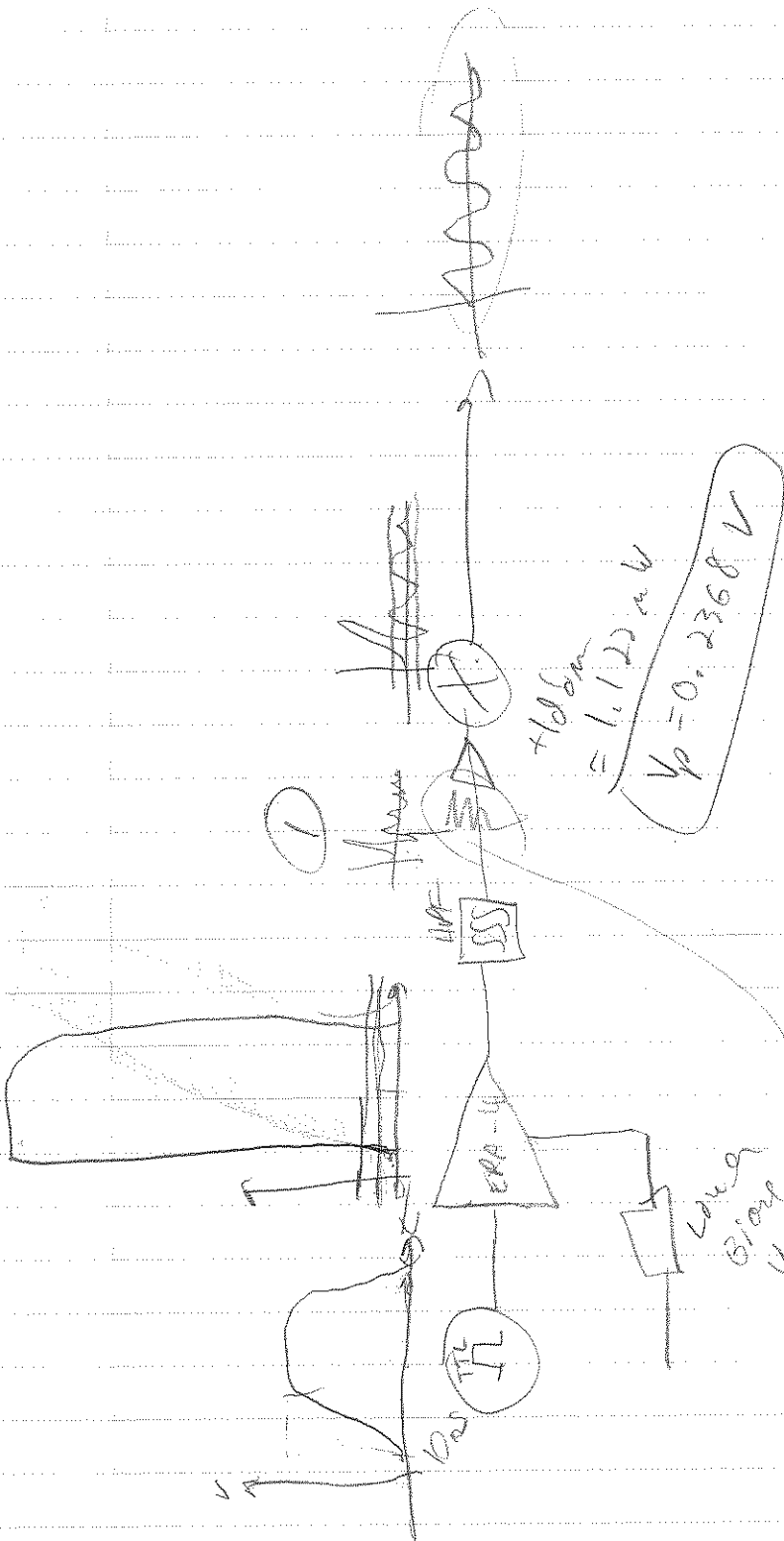

- ① Measure peak Amplitude
- ② Long Amp Bites
- ③ put pads



ECE 480 Project

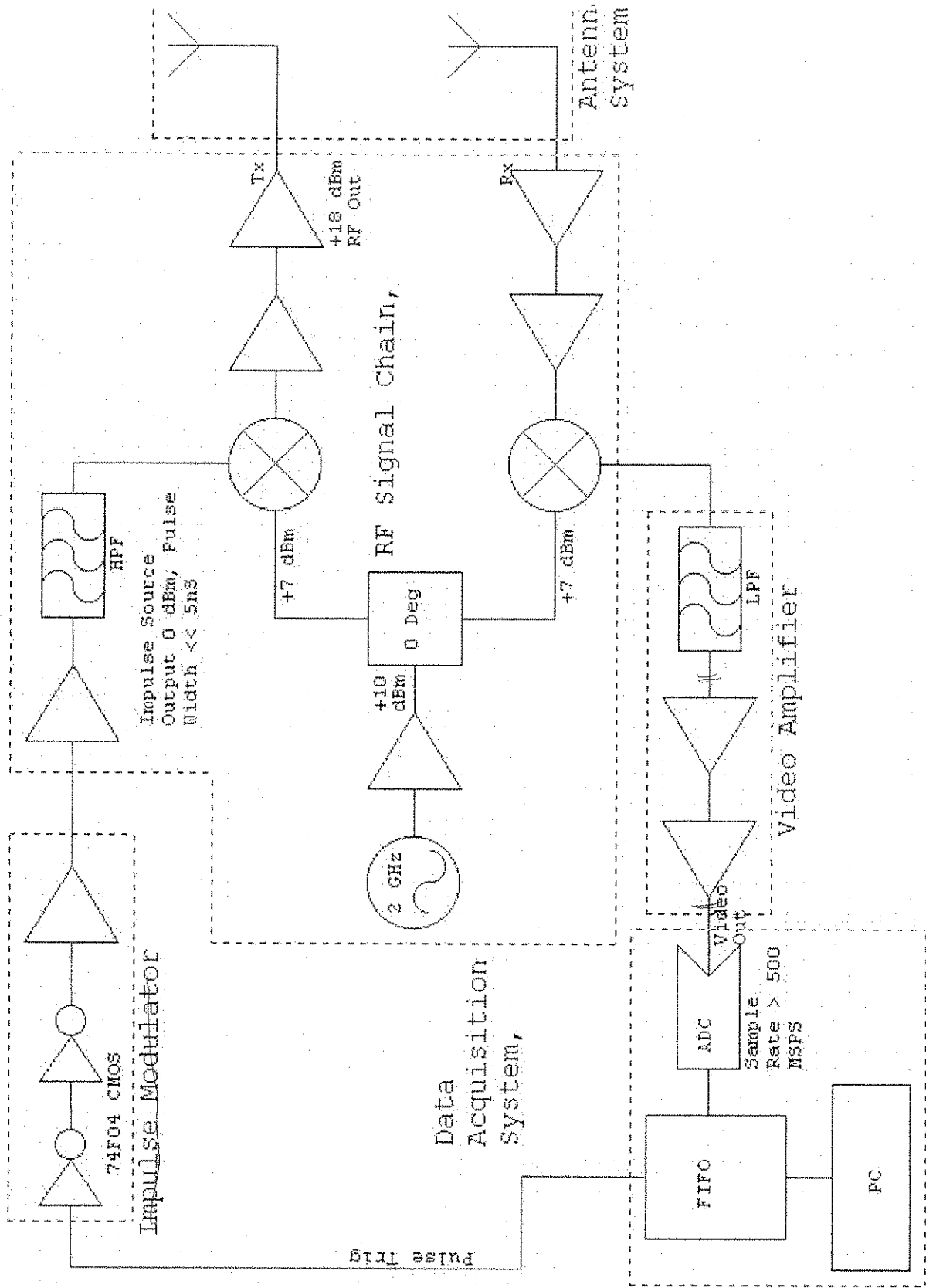

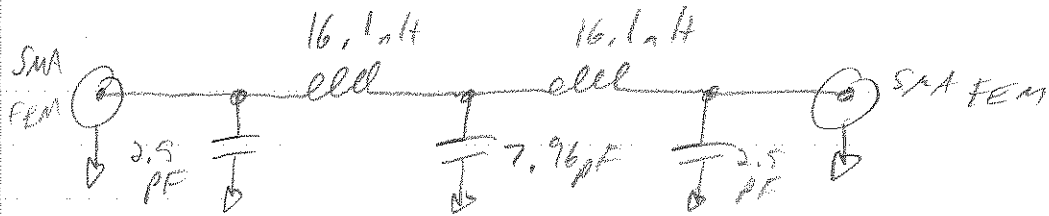


5th order Butterworth
 800 MHz LPF



IF Filter

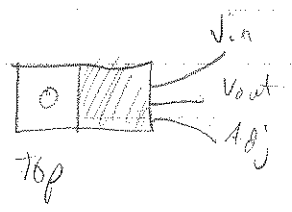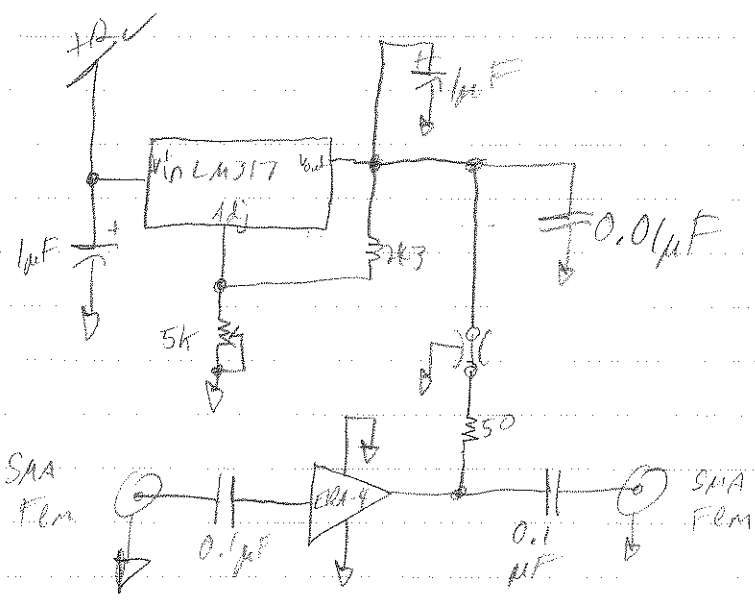



Adjustable Bias
Amp

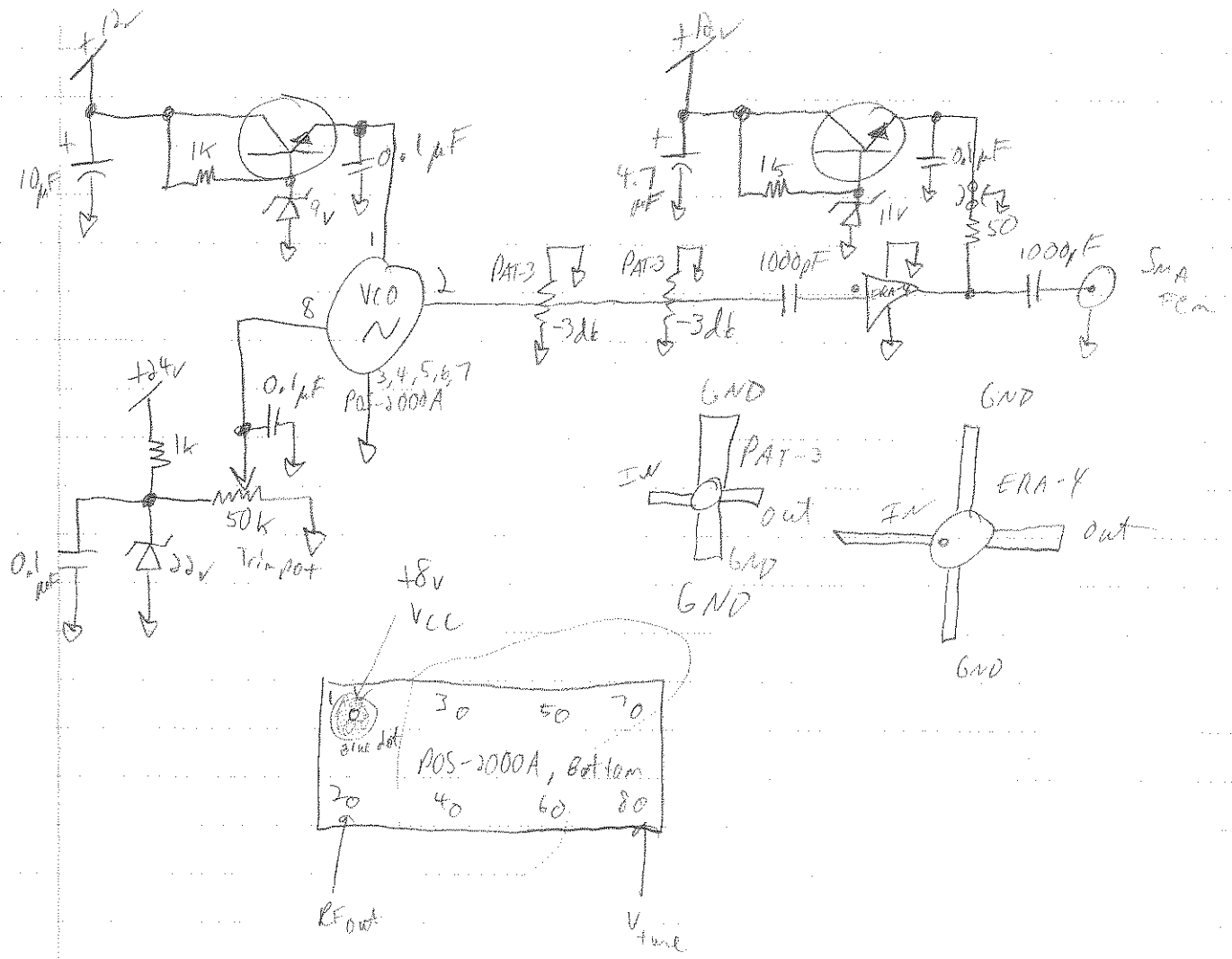

VCO
1.5 - 2 GHz

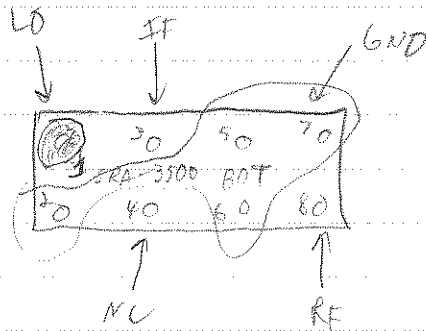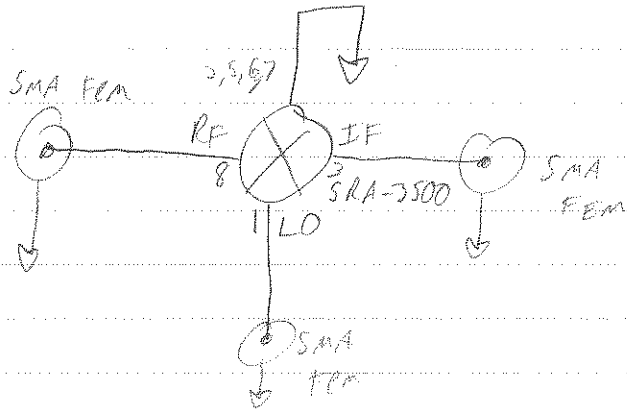

Tx/Rx Mixer

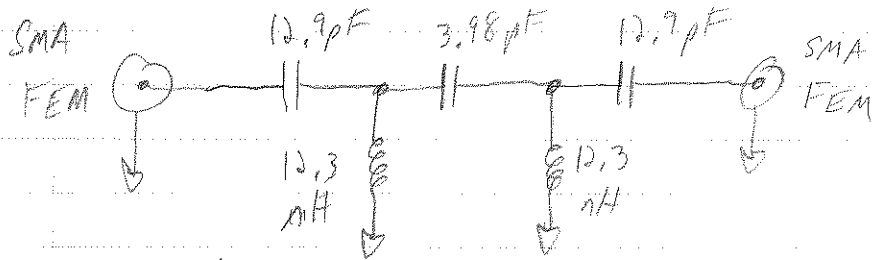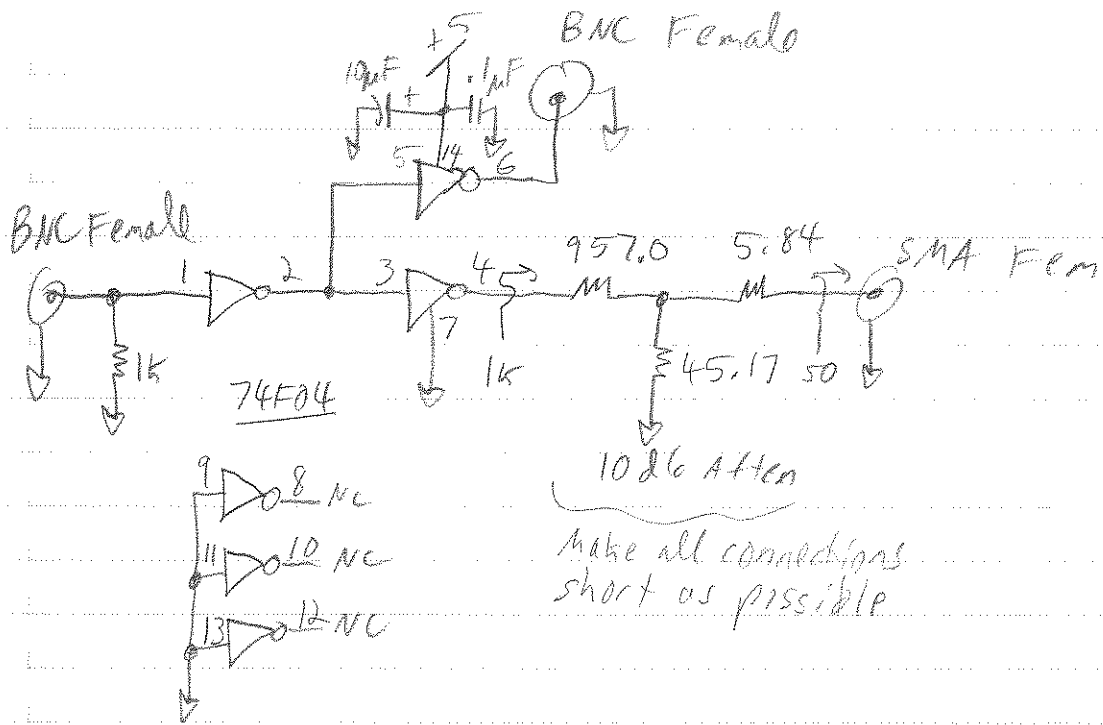


5th order 400 MHz LP
 Butterworth response
 → Build on Microstrip


Impulse Source

Butterworth Filter calculations


→ 400 MHz HP, 5th order

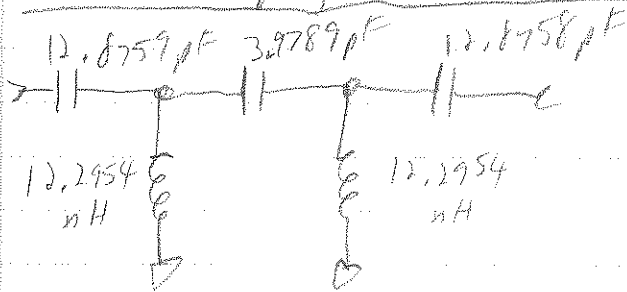


300 MHz HP, 5th order

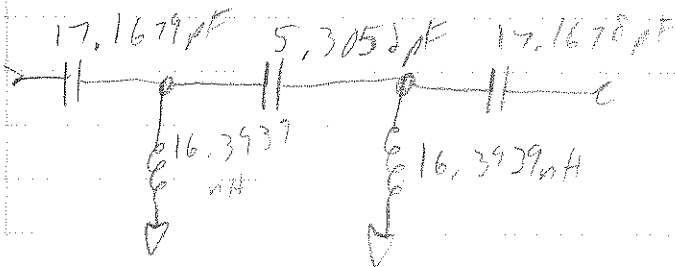

400 MHz HP, 3rd order

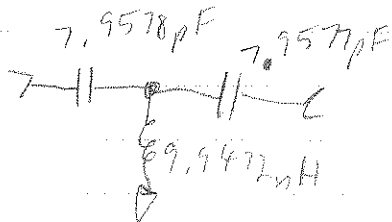

300 MHz HP, 3rd order

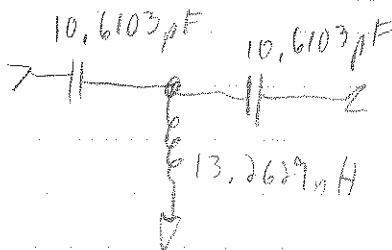

Monday, June 16 2010

SPAC




at Kellogg center

- 2 ZEM-4300
- 30 ERA-4
- 1 ZN2PD-96
- 5 POS-2000A

- Mixer
- Amp
- splitter
- VCO

72.95	159.90
3.85	115.5
69.95	69.95
14.95	74.75
	<hr/>
	480.10

just need 2
just need 10

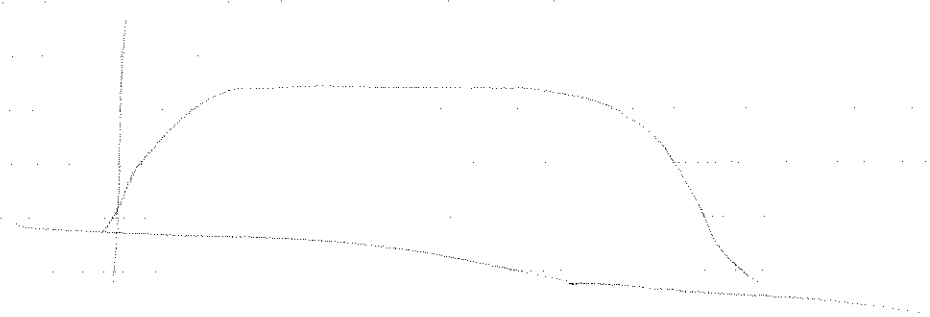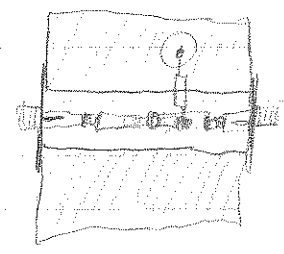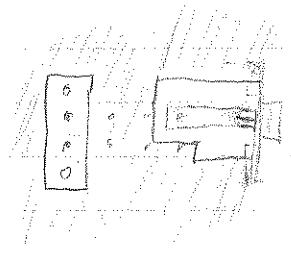

Design Specifications

Carrier freq. 2 GHz

pulse width $\leq 5 \text{ n s}$

Tx power +20 dbm



Coherent Radar structure


Reach of concept. Prototype,
size, power supplies, etc not
considered yet.


Budget

- Transmitter and Receiver - \$400
- Short pulse generator - \$50
- Antennae - \$25
- Video Amplifier - \$25
- Data Acquisition system - \$0
(use existing scopes in Lab)

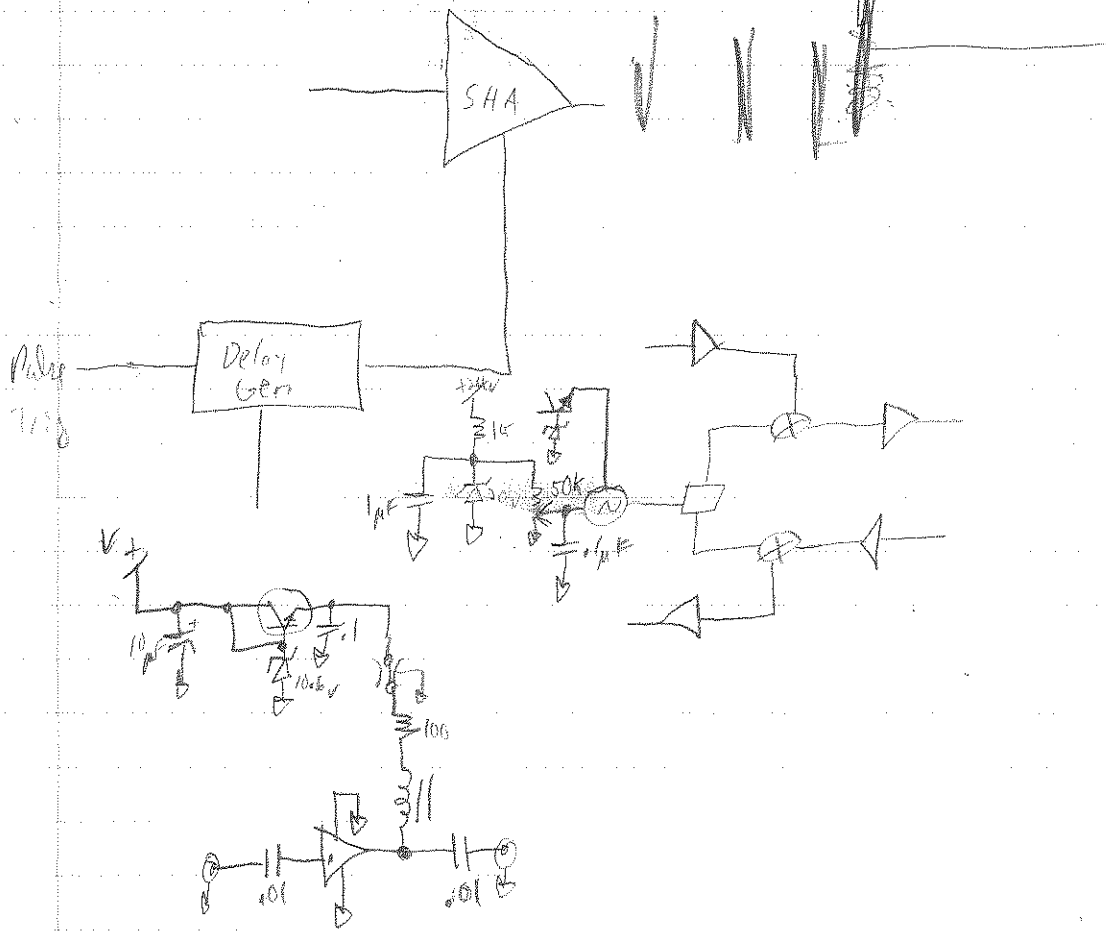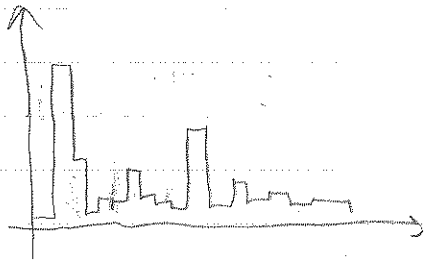Get a project, write a small report
How solder it better.



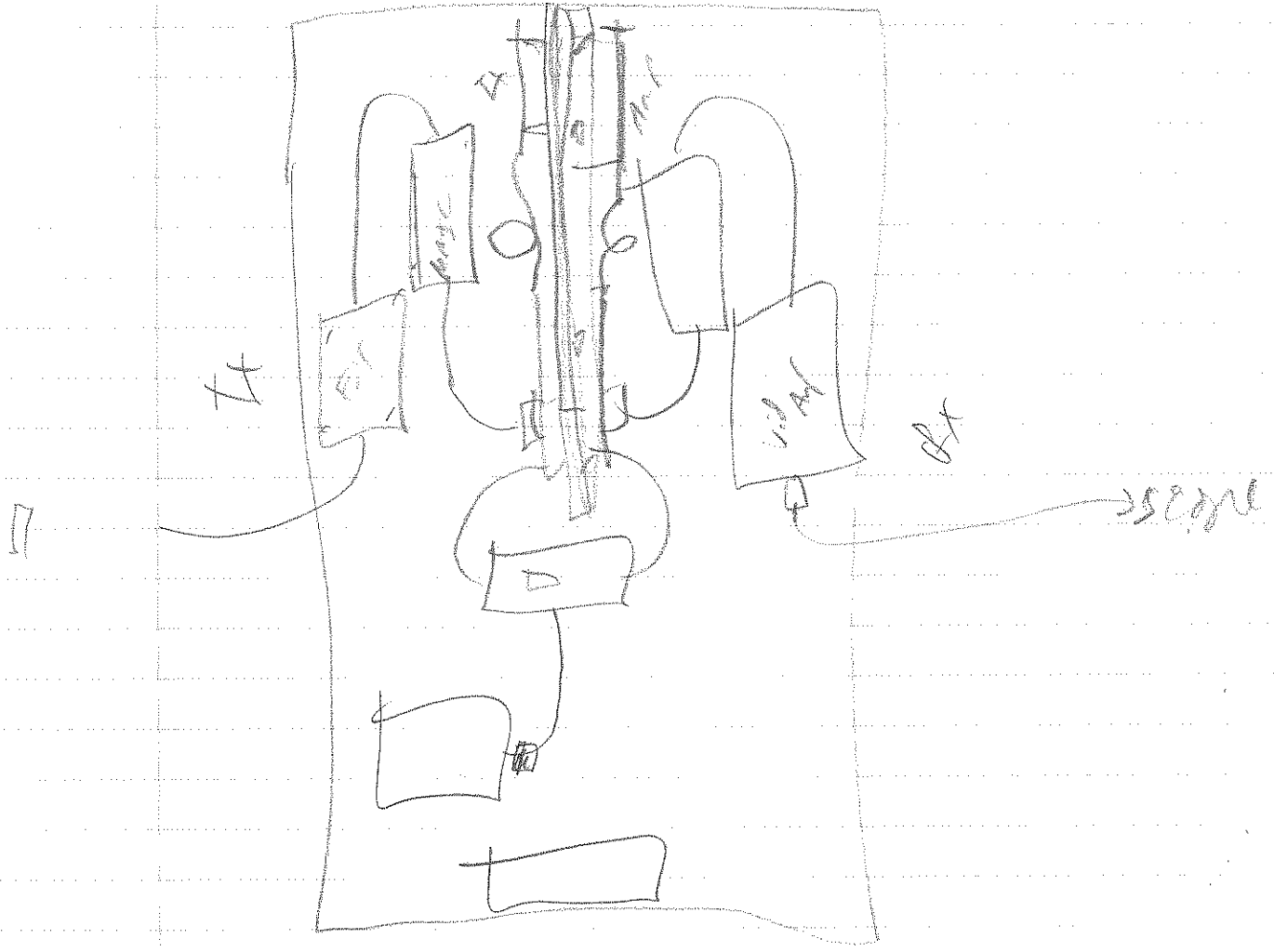

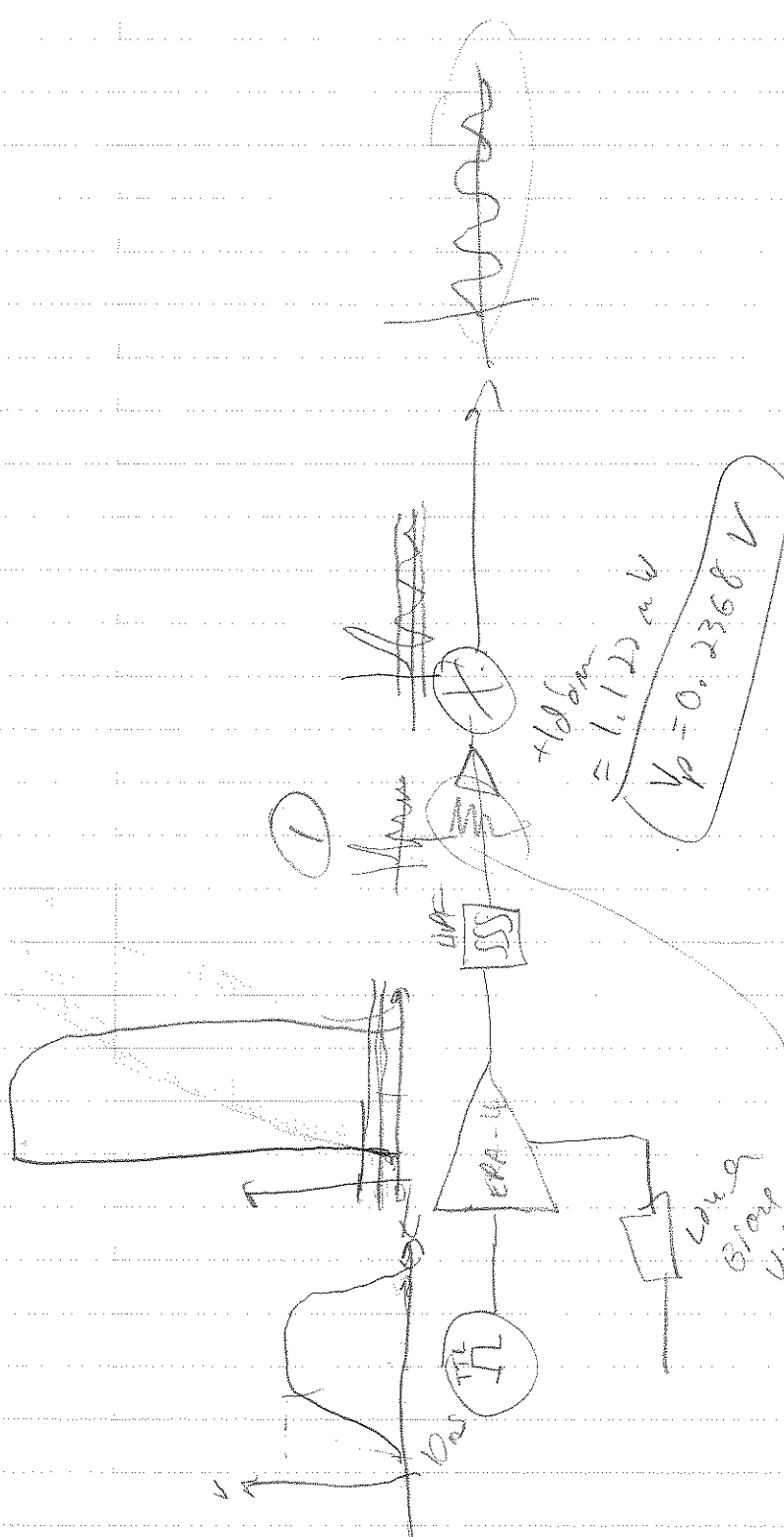

- ① Measure peak A_{100}
- ② Long Avg Bias
- ③ put reads

1.74 GHz = f_{LO}

Circulator attenuation = 30 dB

